
DAY #12

30 DAYS OF VERILOG

AIM – TO IMPLEMENT 4 Bit Multiplier

A **4-bit multiplier** is a circuit that allows you to multiply two binary numbers, each consisting of 4 bits.

1. **Functionality:**

- A 4-bit multiplier takes two 4-bit binary numbers (the **multiplier** and the **multiplicand**) and produces an 8-bit output (the **product**).
- The bit size of the product is equal to the sum of the bit sizes of the multiplier and multiplicand.

2. **Circuit Diagram:**

- The circuit diagram for a 4-bit multiplier typically involves logic gates (such as AND gates, XOR gates, etc.) to perform the multiplication.

3. **Working Principle:**

- The 4-bit multiplier processes each pair of corresponding bits from the multiplier and multiplicand.
- It performs partial multiplications for each bit position and accumulates the results to obtain the final product.


4. **Example:**

- Suppose we want to multiply two 4-bit binary numbers: A=1101 (multiplier) and B=1010 (multiplicand).
- The product 'P' can be calculated as follows:
 - $P = A \times B$
 - $P = 1101 \times 1010$
 - $P = 11110110$ (in binary)
 - $P = 246$ (in decimal)

5. **Applications:**

- 4-bit multipliers are commonly used in digital signal processing, communication systems, and arithmetic circuits.
- They play a crucial role in various electronic devices and systems.

SCHEMATIC –

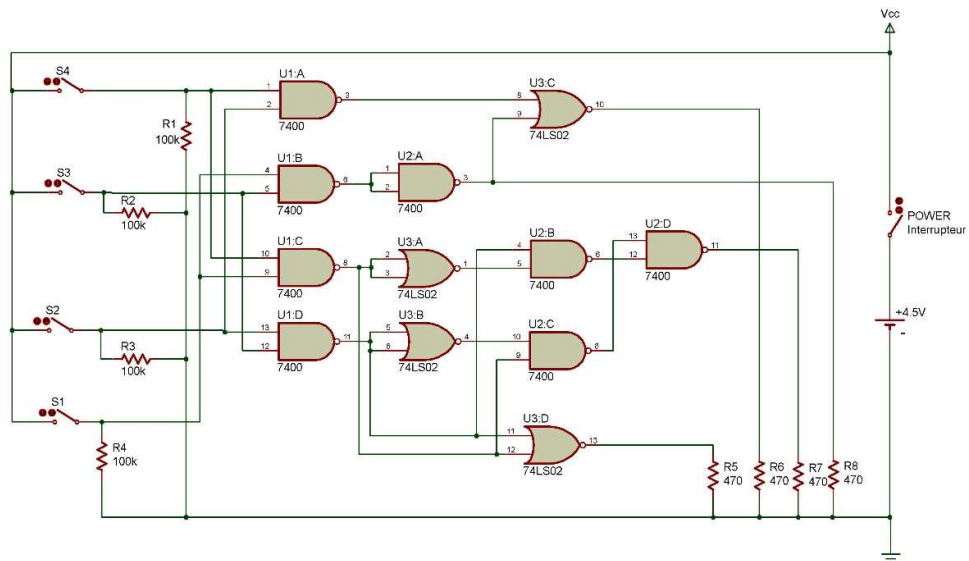

CODE –

```

C:/IntelCity/multiplier/mult4bit.v - Default
Ln#
1  module mult4bit(a, b, p);
2  input [3:0]a,b;
3  wire [3:0]m0;
4  wire [4:0]m1;
5  wire [5:0]m2;
6  wire [6:0]m3;
7
8  wire [7:0]s1,s2,s3;
9
10 output [7:0]p;
11
12 assign m0 = {4{a[0]}} & b[3:0];
13 assign m1 = {4{a[1]}} & b[3:0];
14 assign m2 = {4{a[2]}} & b[3:0];
15 assign m3 = {4{a[3]}} & b[3:0];
16 assign s1= m0 + (m1<<1);
17 assign s2= s1 + (m2<<2);
18 assign s3= s2 + (m3<<3);
19 assign p=s3;
20 endmodule
21

```

WAVEFORM –

