

---

## DAY #20

# ***30 DAYS OF VERILOG***

---

### AIM – TO IMPLEMENT PIPO SHIFT REG.

---

1

The PIPO module implements a Parallel In Parallel Out Register. It takes in these inputs (clk,reset,pipo\_in,load) and an output (pipo\_out).


If reset signal is HIGH, pipo\_out = 0.

If load signal is HIGH, whatever new pipo\_in is coming will be the output.

But, if the load signal is not high, then pipo\_out should show the previously output value. Now what I'm doing is pipo\_out = 0;

What changes can be done, so that when the load signal is not high, then pipo\_out should show the previously output value.

SCHCEMATIC -

 

## CODE –

```
7 // Design Name:
8 // Module Name:  pipo
9 // Project Name:
10 // Target Devices:
11 // Tool versions:
12 // Description:
13 //
14 // Dependencies:
15 //
16 // Revision:
17 // Revision 0.01 - File Created
18 // Additional Comments:
19 //
20 ///////////////////////////////////////////////////////////////////
21 module pipo(q,clk,clr,d);
22 output reg [3:0]q;
23 input clk,clr;
24 input [3:0]d;
25 always @ (posedge clk)
26 if(clr==1)
27 q=4'b0000;
28 else
29 q=d;
30 endmodule
31
```

## WAVEFORM –

