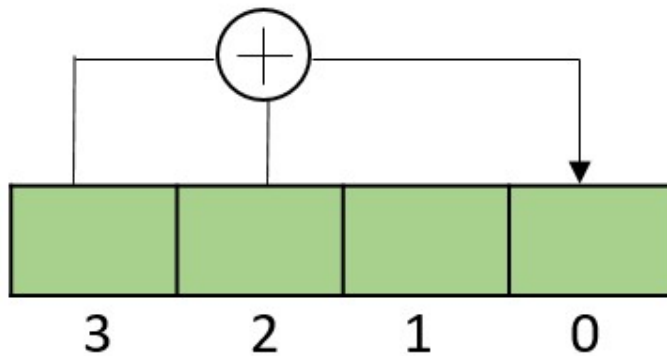

DAY #24

30 DAYS OF VERILOG

AIM – TO IMPLEMENT LINEAR FEEDBACK SHIFT REGISTER

A Linear-feedback shift register (LFSR) is another variation of shift register whose input bit is a linear function (typically XOR operation) of its previous state. It is generally used as a pseudo-random number generator, whitening sequence, pseudo-noise sequence, etc.

The bit positions that act as an input to a linear function to affect the next state are known as taps.



Linear-feedback shift register (LFSR)

At every step,

1. $Q[3] \text{ xor } Q[2]$
2. $Q = Q \ll 1$
3. The result of the XOR operation is fed to the LSB (0th bit)

In the above pseudo-random sequence generator, taps are 4 and 3.

CODE –

```
1 module LFSR(input clk, rst, output reg [3:0] op);  
2     always@(posedge clk) begin  
3         if(rst) op <= 4'hf;  
4         else op = {op[2:0],(op[3]^op[2])};  
5     end  
6 endmodule
```

WAVEFORM-

```
op=xxxx  
op=1111  
op=1110  
op=1100  
op=1000  
op=0001  
op=0010  
op=0100  
op=1001  
op=0011  
op=0110  
op=1101  
op=1010  
op=0101  
op=1011
```