
DAY #11

30 DAYS OF VERILOG

AIM – TO IMPLEMENT 2 Bit COMPARATOR

A **2-bit comparator** is a circuit that compares two 2-bit natural numbers, denoted as A (with bits $A1$ and $A0$) and B (with bits $B1$ and $B0$). The output of the comparator, denoted as S , indicates the relationship between the two numbers:

- If A is greater than B , then $S = 1$.
- Otherwise, if A is less than or equal to B , then $S = 0$.


Comparison Process:

- The circuit compares the bits of the two numbers starting from the most significant bit (MSB) and moving toward the least significant bit (LSB).
- At each bit position, the corresponding bits of A and B are compared.
- If the bit in A is greater than the corresponding bit in B , the output $A > B$ is set to 1, indicating that A is greater than B .
- Similarly, if the bit in B is greater than the corresponding bit in A , the output $A < B$ is set to 1, indicating that A is less than B .
- If the two corresponding bits are equal, the circuit moves to the next bit position and compares the next pair of bits.
- This process continues until all the bits have been compared.

Truth table –

A	B	A>B	A<B	A=B
0	0	0	0	1
0	1	0	1	0
1	0	1	0	0
1	1	0	0	1

BLOCK DIAGRAM –

 

VERILOG CODE –

```
11 // Tool versions:
12 // Description:
13 //
14 // Dependencies:
15 //
16 // Revision:
17 // Revision 0.01 - File Created
18 // Additional Comments:
19 //
20 ////////////////////////////////////////////
21 module comparator(
22     input [1:0] a,b,
23     output alb,aeb,agb
24 );
25     always @(a,b)
26     begin
27         alb=0; aeb=0; agb=0;
28         if(a>b)
29             agb=1;
30         else if (a==b)
31             aeb=1;
32         else alb =1;
33     end
34 endmodule
35
```

WAVE FORM-

