

---

## DAY #4

# 30 DAYS OF VERILOG

---

### AIM – TO IMPLEMENT FULL SUBTRACTOR


A **full subtractor** is a digital logic circuit that performs the subtraction of two binary numbers. It has three inputs: **A**, **B**, and **Borrow In (Bin)**, and two outputs: **Difference (D)** and **Borrow Out (Bout)**. Let's break down how it works:

1. **Inputs:**
  - **A:** Minuend bit
  - **B:** Subtrahend bit
  - **Bin:** Borrow-in bit from the previous stage
2. **Outputs:**
  - **Diff:** Difference bit
  - **Bout:** Borrow-out bit for the next stage


Truth Table –

Input			Output	
A	B	C	Difference	Borrow
0	0	0	0	0
0	0	1	1	1
0	1	0	1	1
0	1	1	0	1
1	0	0	1	0
1	0	1	0	0
1	1	0	0	0
1	1	1	1	1

Schematic –

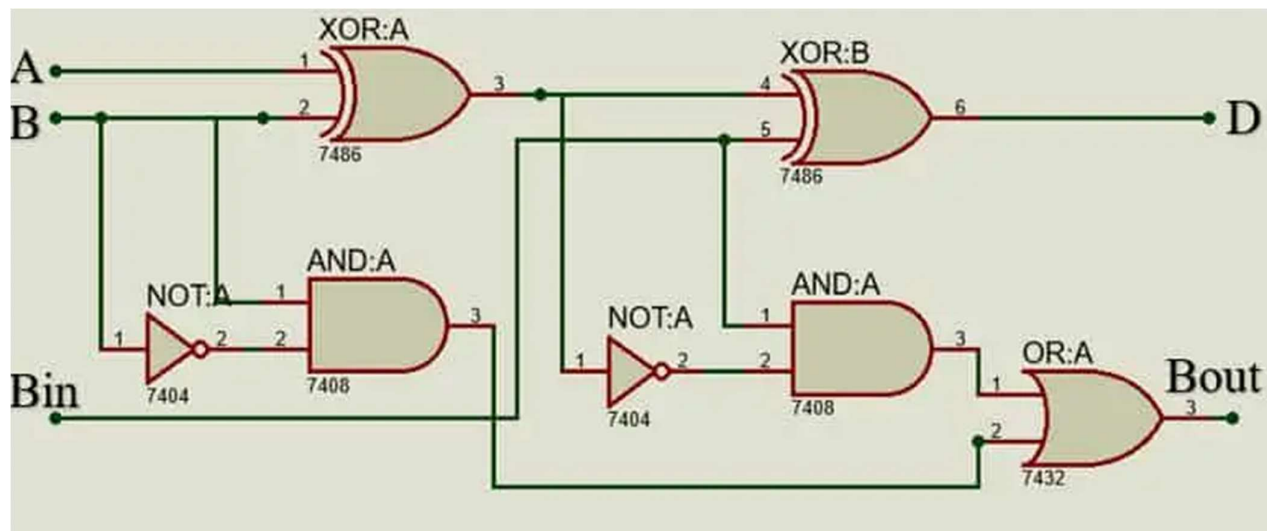

## Verilog Code–

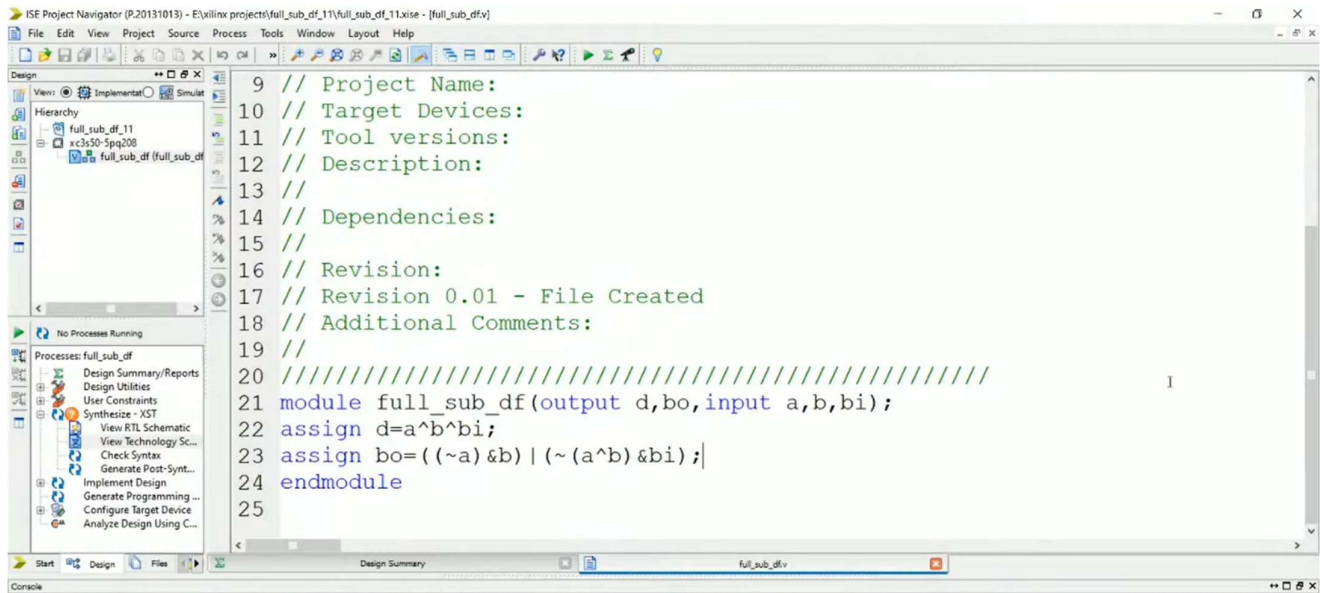

## Waveform –

